
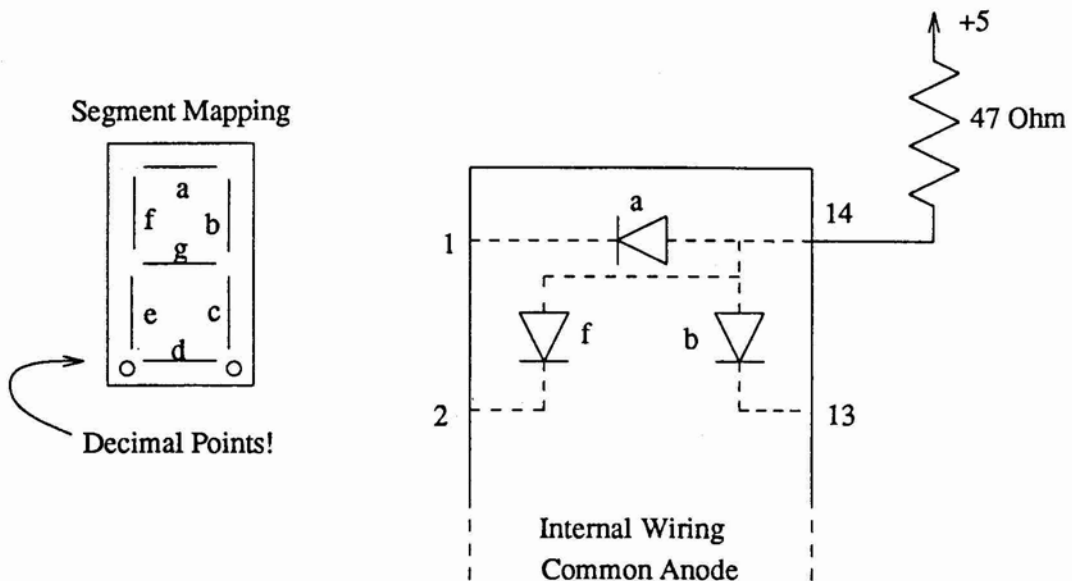


MAN-72 Seven Segment Display

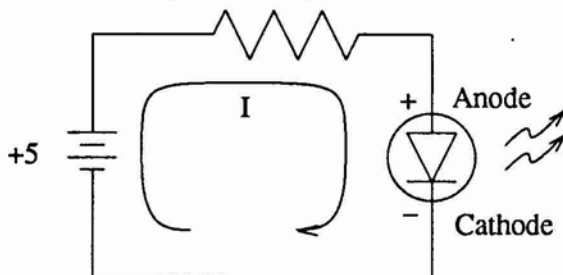

Basic Light Emitting Diode Circuit



If the polarity is reversed
no current will flow and no
light will be emitted.

Pin ¹²	1	2	7	8	10	11	13	14
Segment	a	f	e	d	c	g	b	+5

¹²Some Seven Segment Displays require that additional pins be connected to +5V.